

## Tuned amplifier.


### Syllabus:-

- Introduction
- Classification of small signal tuned amplifier,
- Single tuned amplifier capacitively coupled,
- Tapped single tuned capacitively coupled amplifier,
- Single tuned inductively coupled amplifier,
- Double tuned amplifier.


### 5.1 Introduction:-

- An amplifier which amplifies a selective frequency and rejects all other frequencies is called as tuned amplifier.
- It is an amplifier with tuned or tank ckt. at the collector end called as tuned amplifier.
- As it has narrow bandwidth hence the name narrow band amplifier.
- It uses a parallel tuned ckt. as its load impedance.
- Parallel tuned ckt. has high impedance at resonance & falls sharply as we move away from resonant frequency.


Impedance curve

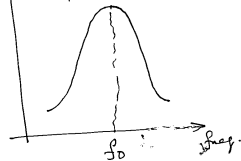

Frequency response of tuned amplifier

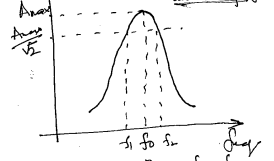

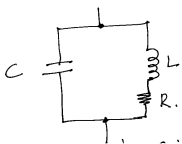- The tuned ckt. or tank circuit is as follows.



$R \rightarrow$  coil resistance (distributed parameter).

single or tuned amplifier will

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (\omega \leftarrow f)$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$\Rightarrow$  Resonant frequency.

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Quality-factor (Q) of the tank circuit.

$$Q = \frac{\text{Voltage drop across } L}{\text{Voltage drop across } R} = \frac{2\pi \left[ \frac{\text{max energy stored per cycle}}{\text{max energy dissipated per cycle}} \right]}$$

$$Q = \frac{V_L}{V_R} = \frac{I_L \cdot X_L}{I_L \cdot R} = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{1}{\omega RC}$$

or Q at resonance.

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Bandwidth

$$BW = \frac{f_0}{Q_0} \text{ Hz.}$$

$$BW = \frac{\omega_0}{Q_0} \text{ rad/sec.}$$

Selectivity. (S)

$$S = \frac{\omega - \omega_0}{\omega_0} = \frac{\omega}{\omega_0} - 1.$$

Parallel resonant circuit has.

$$\rightarrow Z_0 = \frac{L}{RC} \text{ at resonance \& it is } \infty$$

$$\rightarrow I = \frac{V}{Z_0}$$

$$\rightarrow f_0 = \frac{1}{2\pi\sqrt{LC \left( \frac{R}{L} \right)^2}} \approx \frac{1}{2\pi\sqrt{LC}}$$

$$\rightarrow \text{Q-factor } Q = \frac{\omega L}{R} = \frac{1}{\omega RC}$$

amplifier.


→ A resonant circuit is a parallel combination of L & C for adjusting  $f_0$  at Variable Capacitor or a Variable Inductor can be used.

→ In tuned amplifier, harmonic distortion is very small as it selects a single frequency & rejects all other frequencies.

→ If a parallel tuned circuit is applied with a source then the frequency of the applied voltage is equal to the resonant frequency of LC circuit, then the electrical resonance occurs, impedance of the resonant ckt. will be maximum & the line current is minimum & the power factor is unity.

The admittance of Inductive branch is

$$Y_L = \frac{1}{R + j\omega L}$$

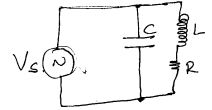

admittance of Capacitive branch is.

$$Y_C = j\omega C$$

$$\text{Total Admittance} = Y_t = Y_L + Y_C = \frac{1}{R + j\omega L} + j\omega C$$

Solving by Rationalizing we get

$$Y_t = \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C$$

$$= \frac{R}{R^2 + \omega^2 L^2} + j\left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2}\right)$$

As we know at Resonance Reactance is zero ( $X=0$ )

$$\omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$$

$$\therefore \omega_0 C = \frac{\omega_0 L}{R^2 + \omega_0^2 L^2}$$

$$RC^2 + \omega_0^2 L^2 C = L$$

Based on the Vlp Signal that has to be amplified tuned amplifiers

are further classified into

(a) Small Signal tuned amplifiers

(b) Large Signal tuned amplifier.

→ As the input signal is small for small signal tuned amplifier the operating point is chosen at the center of the load line hence used in class A mode.

→ As the vlp signal is large for large signal tuned amplifier we used the amplifier in class AB or B or C modes for large collector circuit efficiency. If design using push-pull operation further harmonic distortion will be reduced.

→ As the tuned circuit it self eliminates the harmonic distortion.

→ Small signal tuned amplifiers are further classified as.

(a) Single tuned amplifier

(i) Capacitively Coupled single tuned amplifier.

(ii) Tapped Capacitively Coupled single tuned amplifier.

(iii) Inductively Coupled single tuned amplifier.

(b) Double tuned amplifier.

(c) Stagger tuned amplifier.

→ Single tuned amplifier uses one parallel tuned circuit as the load impedance in each stage and all tuned circuits are independent stages are tuned to the same frequency (when cascaded).

→ Double tuned ckt. is the one which has a inductively coupled two tuned circuit designed for same frequencies.

→ Stagger tuned amplifier is the one which has cascaded single tuned circuits tuned to slightly different frequencies.

→ It's a single-tuned amplifier i.e., it has one tank circuit & the o/p of the amplifier is coupled to the next circuit through a capacitor hence the name capacitively coupled single-tuned amplifier as shown below.

→  $R_1$  &  $R_2$  are biasing elements to make the transistor to be in active mode so that it works like an amplifier.

→  $R_E$  &  $C_E$  provides stabilization.

→  $V_S$  is the source with its internal resistance  $R_i$ .

→ parallel LC forms a tank ckt or tuned circuit.


→  $R$  is the internal resistance of coil  $L$ .

→  $C_o$  forms a coupling capacitor to couple o/p of first stage as the input to the next stage.


→ As the input  $V_S$  is applied the transistor will amplify the signal as it is in active mode & the tuned circuit will select the i/p frequency or at the resonant frequency it offers high impedance & hence the o/p voltage & also the gain will be high for all other frequencies gain gets reduced as we move away from the resonant frequency.

→ To analyze the above circuit we replace our transistor  $Q$  with a hybrid  $\pi$  model rather than hybrid model because the tuned amplifiers are used at radio (high) frequencies.

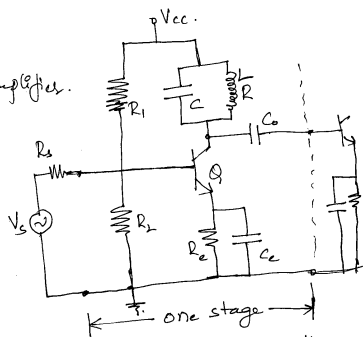
→ To analyze draw the ac. equivalent ckt. & replacing the transistor with hybrid  $\pi$  model & applying miller's theorem to it will be as follows.



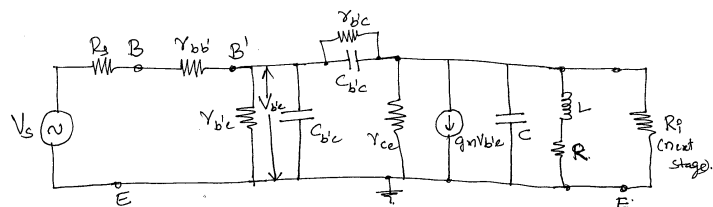circuit, then the equivalent ckt is as follows



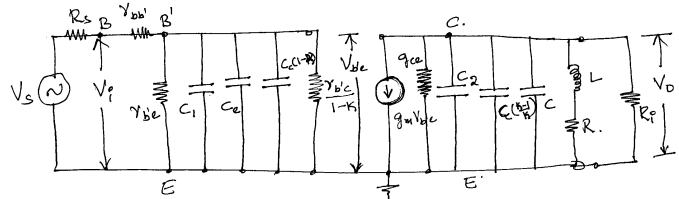→ by applying miller's theorem on to  $C_{be}$  &  $C_{bc}$  gives.




→ Replacing all i/p section capacitance with  $C_S$  & o/p section capacitance with  $C_L$

which are  $C_S = C_1 + C_2 + C_{bc}(1-k)$

$C_L = C_2 + C_{bc}(1/k) + C$

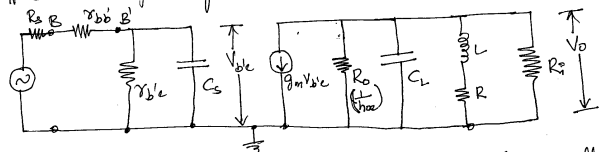→  $C_1$  &  $C_2$  are wiring capacitance or stray capacitances at the i/p & o/p circuits respectively.




→ Converting the series combination of  $L$  &  $R$  into equivalent parallel combination

$$L = R \cdot j\omega L = R \cdot \frac{j\omega L}{1 + j\omega L/R} = \frac{1}{\frac{1}{R} + \frac{j}{\omega L}}$$

$$R \sim R \quad C \cdot \omega L \gg R$$

$$L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L} \approx L \quad [\because \omega^2 L^2 \gg R^2]$$

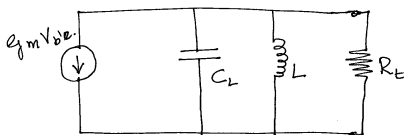Replacing & redrawing the o/p equivalent ckt. we get



$$\text{where } R_t = R_o \parallel R_p \parallel R_i$$

→ Resonant angular frequency  $\omega_0$  is

$$\omega_0 = \frac{1}{\sqrt{LC_L}} \quad \therefore f_0 = \frac{1}{2\pi\sqrt{LC_L}}$$

→ The effective Quality factor or the circuit magnification factor of the entire output circuit at resonance is given as

$$Q_e = \frac{\text{Susceptance of Inductor \& Capacitor } C_L}{\text{Conductance of Shunt Resistance } R_t}$$

$$= \frac{R_t}{\omega_0 L} = \omega_0 R_t C_L$$

→ To define the gain of the amplifier we define o/p voltage  $V_o$  & is given as

$$V_o = -g_m V_{be} \cdot Z$$

where  $Z \Rightarrow$  equivalent impedance of  $R_t, C_L$  &  $L$  of the output circuit.

→ Its admittance is given as  $Y = \frac{1}{Z}$

$$Y = \frac{1}{Z} = \frac{1}{R} + \frac{j}{\omega L} + j\omega C_L$$

$$Y = \frac{1}{R_t} \left[ 1 + \frac{j\omega L}{R_t} + j\omega R_t C_L \right]$$

→ multiply & divide 1st & 3rd terms with  $\omega_0$

$$Y = \frac{1}{R_t} \left[ 1 + \frac{\omega_0 R_t}{j\omega \omega_0 L} + j \frac{\omega \omega_0 R_t C_L}{\omega_0} \right]$$

$$Y = \frac{1}{R_t} \left[ 1 - j \frac{\omega_0}{\omega} \cdot Q_e + j \frac{\omega}{\omega_0} Q_e \right]$$

$$Y = \frac{1}{R_t} \left[ 1 + j Q_e \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

$$\therefore Z = \frac{1}{Y} = \frac{R_t}{1 + j Q_e \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

→ indicating a fractional frequency variation with  $\delta$  which is

$$\delta = \frac{\omega - \omega_0}{\omega_0} = \frac{\omega}{\omega_0} - 1$$

$$\frac{\omega}{\omega_0} = 1 + \delta$$

→ Substituting  $\frac{\omega}{\omega_0}$  in  $Z$  we get

$$Z = \frac{R_t}{1 + j Q_e \left[ (1 + \delta) \frac{1}{1 + \delta} \right]} = \frac{R_t}{1 + j Q_e \left[ \frac{(1 + \delta)^2 - 1}{1 + \delta} \right]}$$

$$= \frac{R_t}{1 + j Q_e \left[ \frac{1 + 2\delta + \delta^2 - 1}{1 + \delta} \right]} = \frac{R_t}{1 + j Q_e \left[ \frac{2\delta + \delta^2}{1 + \delta} \right]}$$

$$= \frac{R_t}{1 + j 2\delta Q_e \left[ \frac{1 + \delta/2}{1 + \delta} \right]} =$$

$$Z = \frac{R_t}{1 + j 2\delta Q_e} \quad [\text{As } \omega \rightarrow \omega_0 \quad \delta \ll 1]$$

$$Z = R_t = R_o \parallel R_p \parallel R_f$$

$$\text{Where } R_p = \frac{\omega_o^2 L^2}{R} = \frac{\omega_o^2 L}{\omega_o C R} = \frac{L}{C R}$$

at resonance

$$R_p = \omega_o L Q_o = Q_o^2 R = Q_o \sqrt{\frac{L}{C}}$$

$$= \omega_o L Q_o = Q_o^2 R = Q_o \sqrt{\frac{L}{C}}$$

$$\therefore V_o = -g_m V_{be} \cdot Z$$

$$\text{as } V_{be} = \frac{V_{be}}{V_{be} + V_{be}} \cdot V_i \quad [\text{neglecting } C_s \text{ \& applying voltage divider rule to } v_p]$$

$$\therefore V_o = -g_m \frac{V_{be}}{V_{be} + V_{be}} \cdot Z \cdot V_i$$

$$\approx -g_m \cdot Z \cdot V_i \quad [\because V_{be} + V_{be} \approx V_{be}]$$

$$A_v = \frac{V_o}{V_i} = -g_m Z$$

$$A_v = -g_m \frac{R_t}{1 + j 2 \delta Q_e}$$

$$|A_v| = \frac{g_m \cdot R_t}{\sqrt{1 + (2 \delta Q_e)^2}}$$

at resonance  $\omega = \omega_o \therefore \delta = 0$

$$\therefore |A_{v_{res}}| = g_m \cdot R_t$$

$$A_{res} = -g_m R_t$$

$$\text{Gain } A_v = A = \frac{A_{res}}{1 + j 2 \delta Q_e}$$

$$\frac{A}{A_{res}} = \frac{1}{1 + j 2 \delta Q_e} \Rightarrow \left| \frac{A}{A_{res}} \right| = \frac{1}{\sqrt{1 + (2 \delta Q_e)^2}}$$

frequency response is as follows.

→ Its gain Bandwidth product is

$$A_{v_{res}} \times \text{Bandwidth}$$

$$GBW = A_{v_{res}} \times BW$$

$$GBW = \frac{g_m R_t}{2\pi R_t C_L} = \frac{g_m}{2\pi C_L}$$

### Tapped Capacitively Coupled Single-tuned amplifier:-

→ This circuit is similar to that of capacitively coupled single tuned amplifier with Inductor in the tank circuit is a tapped Inductor hence the name.

→ By a tapped inductor in tuned circuit the o/p impedance of the CE amplifier & the input impedance of the next stage are made to get matched by which maximum power from output to next stage input is been transferred.

→ The ckt is as shown in the fig. @

→  $R_1, R_2, R_E$  &  $C_E$  are Biasing & Stabilizing elements.

→  $C$  &  $L$  constitute a tank ckt.


→  $V_s$  &  $R_s$  are source & its internal resistance.

→  $C_o$  is coupling capacitor.

→  $R_i$  of the next stage works as load to the first stage.

→ Inductor is a variable inductor or a tapped inductor.

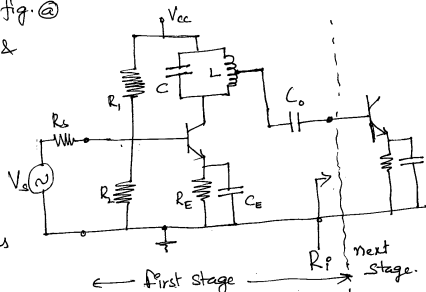→ Position of tapping is adjusted as per the requirement, i.e., as per the output



→ at max power points  $\omega_1 < \omega_o < \omega_2$

$$\frac{A_v}{A_{res}} = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (2 \delta Q_e)^2}}$$

$$\therefore 1 + (2 \delta Q_e)^2 = 2$$

$$(2 \delta Q_e)^2 = 1$$

$$\delta = \pm \frac{1}{2 Q_e}$$

at  $\omega = \omega_1$

$$\delta = -\frac{1}{2 Q_e}$$

$\omega = \omega_2$

$$\delta = +\frac{1}{2 Q_e}$$

Bandwidth  $\Delta \omega = \omega_2 - \omega_1$

add, subtract, multiply & divide with  $\omega_o$

$$= \frac{[\omega_2 - \omega_o + \omega_o - \omega_1] \omega_o}{\omega_o}$$

$$= \left[ \frac{\omega_2 - \omega_o}{\omega_o} + \frac{\omega_o - \omega_1}{\omega_o} \right] \omega_o$$

$$= [\delta + \delta] \omega_o = 2 \delta \omega_o$$

$$\delta = \frac{1}{2 Q_e}$$

$$\therefore BW = \omega_2 - \omega_1 = \frac{2 \omega_o}{2 Q_e} = \frac{\omega_o}{Q_e}$$

$$\text{Bandwidth} = \frac{\omega_o}{\omega_o R_t C_L} = \frac{1}{R_t C_L} \text{ Rad/sec.}$$


In Hertz

$$\text{Bandwidth} = f_2 - f_1 = \frac{1}{\pi R_t C_L} \text{ Hz}$$

→ as when input signal is applied as in the circuit, it will amplify the signal & the tuned circuit will select the frequency & under resonant frequency the impedance offered will be maximum due to which the o/p voltage will be maximum, hence gain will also be maximum.

→ As this is a tapped circuit the tapping is adjusted for maximum power transfer hence the power transferred will be more than to that of the previous circuit hence the gain is improved due to impedance matching by tapped inductor.

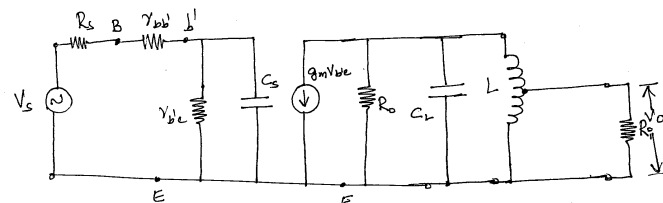→ In order to analyze the above circuit first an ac equivalent is drawn and the transistor is replaced by a hybrid  $\pi$  model. Since these amplifiers are used at radio (high) frequencies and applying Miller's theorem on  $C_{be}$  &  $V_{be}$  we get the simplified ckt. as below.




Equivalent circuit after applying miller's & combining the capacitances.

$$C_s = C_1 + C_2 + C_c(1-k) \quad ; \quad C_L = C_2 + C + C_c\left(\frac{1-k}{k}\right)$$

→ Simplified output circuit can be redrawn by splitting the inductor  $L$  into  $L_1$  &  $L_2$  where  $L_1 = nL$  &  $L_2 = (1-n)L = (1-n)L = L - nL = L - L_1$
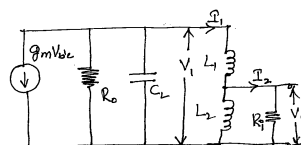
$$\therefore L_1 + L_2 = L \text{ \& the ckt. is}$$



$$V_1 = j\omega L I_1 - j\omega(L_2 + M)I_2 \rightarrow (1)$$

$$0 = -j\omega(L_2 + M)I_1 + (R_1 + j\omega L_2)I_2 \rightarrow (2)$$

→ Where M is mutual inductance between  $L_1$  &  $L_2$

→ The equations are written by neglecting the coil resistance R.

Solving (1) & (2)

$$0 = -j\omega(L_2 + M)I_1 + (R_1 + j\omega L_2)I_2$$

$$\therefore I_2 = \frac{j\omega(L_2 + M)}{R_1 + j\omega L_2} \cdot I_1 \rightarrow (3)$$

Sub (3) in (1)

$$\therefore V_1 = j\omega L I_1 - j\omega(L_2 + M) \cdot \frac{j\omega(L_2 + M)}{R_1 + j\omega L_2} \cdot I_1$$

$$V_1 = I_1 \left( j\omega L + \frac{\omega^2 L_2^2 + M^2}{R_1 + j\omega L_2} \right)$$

$$\therefore I_1 = \frac{V_1 (R_1 + j\omega L_2)}{j\omega L (R_1 + j\omega L_2) + \omega^2 (L_2 + M)^2}$$

→ Impedance offered by the coil along the resistance  $R_1$  can be written as:

$$Z_1 = \frac{V_1}{I_1} = \frac{j\omega L (R_1 + j\omega L_2) + \omega^2 (L_2 + M)^2}{R_1 + j\omega L_2}$$

$$= j\omega L + \frac{\omega^2 (L_2 + M)^2}{R_1 + j\omega L_2}$$

→ At operating frequencies  $\omega L_2 \gg R_1$ , hence neglecting  $\omega L_2$  in denominator we get:

$$Z_1 = j\omega L + \frac{\omega^2 (L_2 + M)^2}{R_1}$$

$R_{eq}$

Substituting  $R_{eq}$  we get:


$$R_{op} = \frac{\omega_0^2 L^2 R_1}{\omega_0^2 L^2 (1-n) + \sqrt{(n-n^2)}}$$

$$\frac{R_1}{R_{op}} = [(1-n) + \sqrt{(n-n^2)}]^2$$

$$\therefore (1-n) + \sqrt{(n-n^2)} = \pm \sqrt{\frac{R_1}{R_{op}}}$$

→ This above equation states about the tapping of transformer coil that has to be done as per op resistance & load resistance  $R_L$  for max power transfer.

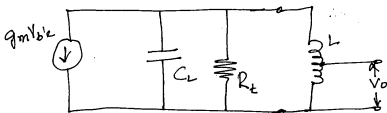→ The equivalent circuit of above figure is as follows



$$\text{where } \frac{1}{R_t} = \frac{1}{R_0} + \frac{1}{R_p} + \frac{1}{R_{ip}}$$

& effective Quality factor is given as  $Q_e = \frac{R_t}{\omega_0 L}$

& the resonant frequency is given as  $f_0 = \frac{1}{2\pi\sqrt{L C_L}}$

→ under matched condition  $R_t = \frac{R_{op}}{2}$   $\therefore R_t = R_{op} \parallel R_{ip}$  & matched condition  $R_{op} = R_{ip}$

$$\therefore Q_e = \frac{R_{op}}{2\omega_0 L}$$

$$R_{op} = 2\omega_0 Q_e L = \frac{R_0 R_p}{R_0 + R_p} \quad (\text{from fig})$$

$$\therefore 2\omega_0 Q_e L = \frac{R_0 \omega_0 Q_e L}{R_0 + \omega_0 Q_e L}$$

$$\rightarrow \text{Solving for } L \text{ we get } \Rightarrow 2Q_e = \frac{R_0 R_0}{R_0 + \omega_0 Q_e L}$$

the length of winding space in the coil is small in comparison with its diameter.

$$\therefore M = k\sqrt{L_1 L_2} = k\sqrt{nL \cdot (1-n)L} = kL\sqrt{(n-n^2)}$$

as  $k=1$ .

$$M = L\sqrt{(n-n^2)}$$

Substituting  $Z_1$  we get:

$$Z_1 = j\omega L + \frac{\omega^2 [(1-n)L + L\sqrt{(n-n^2)}]^2}{R_1}$$

→ From the equation it can be seen that  $Z_1$  is a combination of Inductance L in series with a resistance say  $R_{eq}$ .


$$\text{Where } R_{eq} = \frac{\omega^2 L^2 [(1-n) + \sqrt{(n-n^2)}]^2}{R_1}$$

$$\therefore Z_1 = j\omega L + R_{eq}$$

This series combination can be resolved into equivalent parallel combination with Inductance L in parallel with  $R_{eq}$

$$\text{where } R_{ip} = \frac{\omega^2 L^2}{R_{eq}}$$

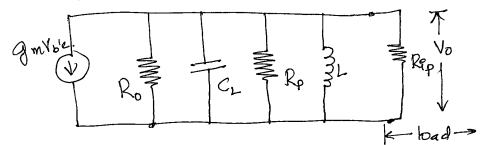→ By this equivalent circuit can be drawn as:



where  $R_p = \frac{\omega^2 L^2}{R}$ ;  $R \rightarrow$  Coil resistance.

→ As  $R_{ip}$  works as a load, under resonance maximum power will transfer if  $R_{ip} = R_0 \parallel R_p = R_{op}$

$$\text{here } R_p = \frac{\omega_0^2 L^2}{R} = \omega_0 L \cdot Q_0$$

$$\frac{1}{2\omega_0 Q_0 Q_e} = \frac{R_0}{\omega_0} \left[ \frac{1}{Q_e} - \frac{1}{Q_0} \right]$$

→ This value of L defines maximum transfer of power & also 3dB bandwidth as defined by  $Q_e$ .

→ Voltage gain can be defined from output voltage which is  $(1-n)$  times the voltage developed across the complete coil, which is

$$V_o = -g_m V_{be} \cdot Z(1-n)$$

$$V_o = -g_m V_i \frac{r_{be}}{r_{be} + r_{ie}} \cdot Z(1-n)$$

$$A_v = \frac{V_o}{V_i} = -g_m \frac{r_{be}}{r_{be} + r_{ie}} \cdot \frac{R_t}{1 + j2\delta Q_e} (1-n)$$

$$\therefore A_v \approx -g_m \cdot \frac{R_t}{1 + j2\delta Q_e} (1-n) = A$$

at resonance as  $\omega = \omega_0 \Rightarrow \delta = 0$

$$\therefore A_{res} \approx -g_m \cdot R_t (1-n)$$

$$\frac{A}{A_{res}} = \frac{1}{1 - j2\delta Q_e}$$

$$\left| \frac{A}{A_{res}} \right| = \frac{1}{\sqrt{1 + (2\delta Q_e)^2}}$$

→ It's similar to that of capacitively coupled but the only variation lies in effective Quality factor  $Q_e$

→ at half power points  $\left| \frac{A}{A_{res}} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (2\delta Q_e)^2}}$

$$\therefore \sqrt{2} = \sqrt{1 + (2\delta Q_e)^2}$$

$$\delta = \pm \frac{1}{2Q_e}$$

at  $\omega = \omega_1$

$$\delta = -\frac{1}{2Q_e}$$

$\omega = \omega_2$

$$\delta = +\frac{1}{2Q_e}$$

$$\therefore \text{Bandwidth} = \omega_2 - \omega_1$$

multiply, divide, add & Subtract  $\omega_0$  to bandwidth.

$$BW = \frac{\omega_2 - \omega_0 + \omega_0 - \omega_1}{\omega_0} \cdot \omega_0$$

$$= \left[ \frac{\omega_2 - \omega_0}{\omega_0} + \frac{\omega_0 - \omega_1}{\omega_0} \right] \omega_0$$

$$= [\delta + \delta] \omega_0 = 2\delta \omega_0$$

$$\text{as } \delta = \frac{1}{2Q_e} \text{ at cutoff.}$$

$$BW = \omega_2 - \omega_1 = \frac{2\omega_0}{2Q_e} = \frac{\omega_0}{Q_e}$$

$$\therefore BW = \frac{\omega_0}{\omega_0 R_e C_L} = \frac{1}{R_e C_L}$$


Under matched condition  $R_t = \frac{R_{op}}{2}$

$$\therefore \text{Bandwidth} = \frac{2}{R_{op} C_L} \text{ Rad/sec}$$

Condition in next is given as.

$$\text{Band width} = f_2 - f_1 = \frac{2}{2\pi R_{op} C_L} = \frac{1}{\pi R_{op} C_L} \text{ Hz.}$$

→ The frequency response is as follows.

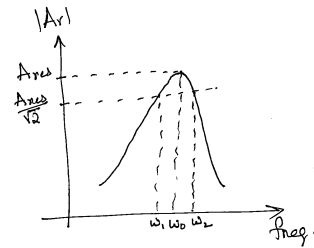

Gain Bandwidth product

$$GBP = A_{v0} \times \text{Bandwidth}$$

$$= \frac{g_m R_t (1-n)}{2\pi R_t C_L} \quad \text{[Matched Condition } R_t = \frac{R_{op}}{2}]$$

$$GBP = \frac{g_m (1-n)}{2\pi C_L}$$

→ This is a single-tuned amplifier whose output signal is coupled to the next stage through an inductor hence the name.

→ It is also called as Transformer Coupled single-tuned amplifier since the tank circuit inductor forms the primary of the transformer and the coupling inductor is called as secondary of the transformer.

→ The secondary of the transformer is connected to the next stage input impedance which works as a load to the first circuit and the circuit is as shown below.

→  $R_1, R_2, R_E, C_E$  forms the biasing & stabilizing network.

→  $V_s$  is a source with its internal resistance  $R_s$ .


→  $L$  &  $C$  forms the tank circuit.

→  $L$  &  $L_2$  forms a transformer for coupling the output signal of first stage to the input of next stage whose input resistance is  $R_i$  which is represented as a load  $R_L$  shown by dotted line.


→ As per the tank circuit's resonant frequency the gain is maximum at  $\omega_0$  & for other frequencies the gain falls rapidly.

→ This signal is coupled through another coil  $L_2$  & the turns ratio of transformer is chosen in such a way that the output impedance gets matched with the load impedance so that maximum power transfer occurs from source to load.

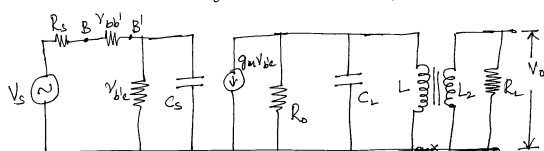→ Analysis can be done by drawing an ac equivalent & replacing the transistor by its high frequency equivalent model i.e., hybrid  $\pi$  model & apply the miller's theorem & resolving then the ckt. appears in this fashion as below.



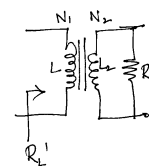→ As we know the transformer's primary inductor is  $L$  & secondary inductor is  $L_2$ .




$R_s'$  is resistance obtained from primary to the load & is given as.

$$R_s' = \frac{1}{n^2} \cdot R_L$$

where  $n$  is  $N_1/N_2$ .

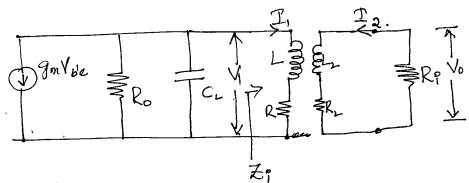→ Redrawing the o/p circuit including the coil resistances



Applying KVL to primary & secondary winding

$$V_1 = I_1 Z_{11} + I_2 Z_{12}$$

$$0 = I_1 Z_{21} + I_2 Z_{22}$$

$$\left. \begin{aligned} \text{where } Z_{11} &= R_1 + j\omega L \\ Z_{12} &= Z_{21} = j\omega M \\ Z_{22} &= R_2 + R_L + j\omega L_2 \end{aligned} \right\}$$

→ Solving the equations we get

$$I_1 = \frac{V_1 \cdot Z_{22}}{Z_{11} Z_{22} - Z_{12}^2}$$

$$\therefore \text{Impedance } Z_i = \frac{V_1}{I_1} = Z_{11} - \frac{Z_{12}^2}{Z_{22}}$$

$$Z_i = (R_1 + j\omega L) + \frac{\omega^2 M^2}{R_2 + R_L + j\omega L_2}$$

$R_2$  is generally greater than  $R_L$  &  $\omega L_2$


$$\therefore Z_i = R_1 + j\omega L + \frac{\omega^2 M^2}{R_i}$$

Primary.

→ If  $M$  is large then  $R \ll \frac{\omega^2 M^2}{R_f}$

$$Z_p \approx j\omega L + \frac{\omega^2 M^2}{R_f}$$

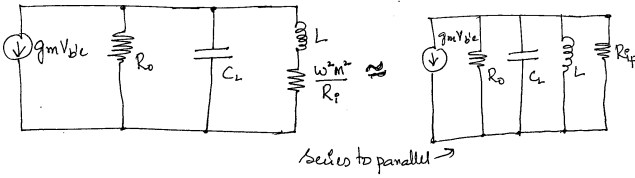→ Now by this  $Z_p$  which is a series combination of  $L$  &  $\frac{\omega^2 M^2}{R_f}$  the o/p circuit can be redrawn as.



$$\therefore R_p = \frac{\omega^2 L^2}{\frac{\omega^2 M^2}{R_f}} = \left(\frac{L}{M}\right)^2 R_f$$

for maximum power transfer  $R_o = R_p = \left(\frac{L}{M}\right)^2 R_f$

→ which says for the given load of  $R_f$ , the desired value of  $M$  for maximum transfer of power happens.


→ as we know  $M = k\sqrt{L_1 L_2}$  → Sub in  $R_o$

$$R_o = \left(\frac{L}{M}\right)^2 R_f = \frac{L}{k^2 L_2} R_f$$

→ as per  $R_o$  &  $R_f$ ,  $L$ ,  $L_2$  &  $k$  are chosen.

→ The final equivalent o/p can be drawn as

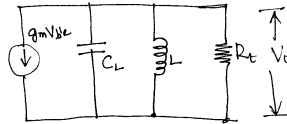Where  $R_t = R_o \parallel R_p$   
 $\therefore Q_o = \frac{R_t}{\omega L}$



$$\omega = \omega_o \Rightarrow \delta = 0$$

$$\therefore A_{res} \approx -g_m \cdot R_t R_f \frac{Z_{21}}{Z_{11}Z_{22} - Z_{12}^2}$$

$$\frac{A}{A_{res}} = \frac{1}{1+j2\delta Q_o} \Rightarrow \left| \frac{A}{A_{res}} \right| = \frac{1}{\sqrt{1+4\delta^2 Q_o^2}}$$

→ Its relative response can be plotted by taking  $\delta V_s A/A_{res}$  as below.

→ As  $Q$  increases bandwidth decreases.

→ gain is been improved due to perfect matching of impedance

→ 3dB bandwidth.


$$Q_o = \frac{\omega_o}{BW}$$

$$\text{as we know } Q_o = \frac{R_t}{\omega_o L} = \frac{R_o}{2\omega_o L}$$

$$\frac{\omega_o}{BW} = \frac{R_o}{2\omega_o L}$$

$\therefore$  Bandwidth  $BW$  is directly proportional to  $L$ .

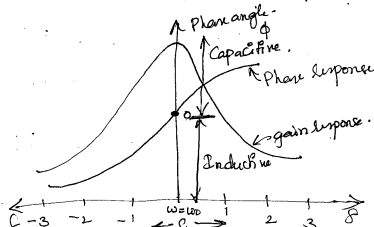→ Reactance curve for different  $\delta$  is plotted as below.



$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

Under matched condition  $R_t = \frac{R_o}{2}$  [ $\therefore R_o = R_{fp}$ ]

$$\therefore Q_o = \frac{R_o}{2\omega_o L}$$

$$R_o = 2Q_o \omega_o L$$

→ gain of the circuit can be obtained by solving KVL eq's.

$$V_1 = I_1 Z_{11} + I_2 Z_{12}$$

$$0 = I_1 Z_{21} + I_2 Z_{22}$$

by solving

$$I_2 = \frac{V_1 \cdot Z_{21}}{Z_{21}^2 - Z_{11}Z_{22}}$$

→ from the fig

$$V_o = -I_2 R_f$$

$$= -V_1 \cdot R_f \cdot \frac{Z_{21}}{Z_{21}^2 - Z_{11}Z_{22}}$$

$$\therefore V_1 = -g_m V_{be} \cdot Z$$

$$Z = \frac{R_t}{1+j2\delta Q_o}$$

$$\therefore V_o = +g_m V_{be} \cdot R_t \cdot R_f \cdot \frac{Z_{21}}{1+j2\delta Q_o \cdot Z_{21}^2 - Z_{11}Z_{22}}$$

$$V_o = -g_m \frac{V_{be}}{r_{be} + r_{be}} \cdot V_i \cdot \frac{R_t R_f}{1+j2\delta Q_o} \cdot \frac{Z_{21}}{Z_{11}Z_{22} - Z_{12}^2}$$

$$A = \frac{V_o}{V_i} \approx -g_m \frac{R_t R_f}{1+j2\delta Q_o} \cdot \frac{Z_{21}}{Z_{11}Z_{22} - Z_{12}^2}$$

→ As this circuit is a combination of two tuned circuit hence the name double tuned amplifier.

→ It is a single-tuned amplifier with wider bandwidth.

→ both the tuned circuits are designed for same resonant frequency & the circuit is as shown below.

→  $R_i, R_L, R_E$  &  $C_E$  forms a biasing & stabilizing elements for transistor (BJT)


→  $V_s$  &  $R_s$  are source & its internal resistance.

→  $C$  &  $L$  forms one tuned circuit.

→  $L_2$  &  $C_2$  forms the 2<sup>nd</sup> tuned circuit.

→  $L$  &  $L_2$  forms a transformer for

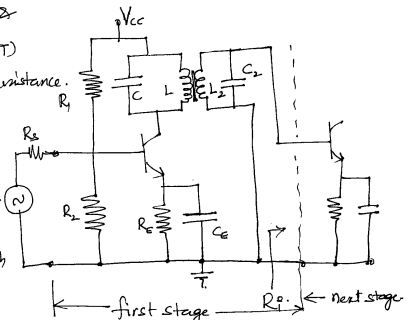
Power transfer from primary to the secondary is, on to its load which is the input resistance of next stage  $R_i$ .



→ As the transistor is in active mode it works like an amplifier & as per the resonant frequency of tank circuit, it amplifies the resonant signal frequency with maximum gain & the gain reduces as we move away from resonant frequency.


→ To analyse we go for drawn an a.c. equivalent & replace the transistor with its hybrid  $\pi$  model as these circuits are used for high (radio) frequencies.

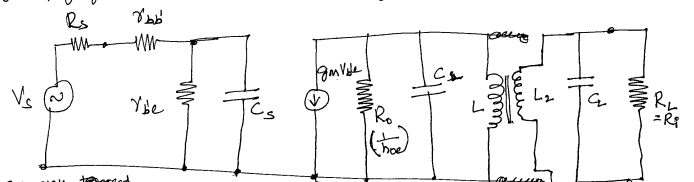→ By applying miller's theorem & analysing for reduced network.




→ Redrawing the output circuit in a simplified form it is as follows

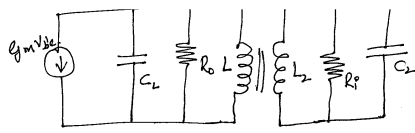→ Redrawing the output circuit in a simplified form it is as follows




Equivalent output circuit

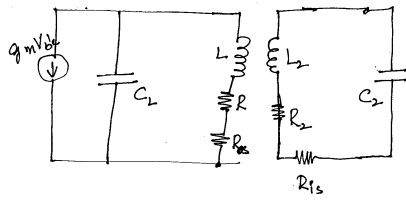
→ Convert the parallel combination of \$R\_o\$ & \$L\$ along with \$L\_2\$ & \$R\_i\$ in series equivalent series as below.



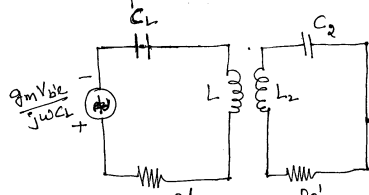- \$R\_{os}\$ is equivalent series resistance of \$R\_o \parallel L\$
- \$R\_{is}\$ is equivalent series resistance of \$R\_i \parallel L\_2\$
- \$R\$ & \$R\_2\$ are internal resistances of \$L\$ & \$L\_2\$.
- Now combining the resistances & converting a network source into thevenin's equivalent. we get:



Modified equivalent circuit.

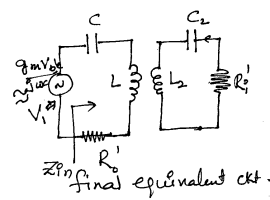

- \$R\_o' = R\_{os} + R\$ ; \$R\_i' = R\_{is} + R\_2\$
- The impedance \$Z\_{in}\$ looking from primary we get \$Z\_{in}\$ as

$$Z_{12} = Z_{21} = j\omega M \quad \& \quad Z_{22} = R_i' + j(\omega L_2 - \frac{1}{\omega C_2})$$

$$Z_{11} = R_o' \quad \& \quad Z_{22} = R_i'$$

$$Z_{12} = j\omega M_c$$

→ Substituting these values of \$Z\_{11}\$, \$Z\_{22}\$ & \$Z\_{12}\$ in \$I\_2\$ gives a relation of maximum power transfer at resonance.

$$I_{2max} = -j \frac{V_1 \omega_0 M_c}{R_o' R_i' + \omega_0^2 M_c^2}$$

Substitute \$\omega M\_c\$ as \$\sqrt{R\_o' R\_i'}\$ we get

$$I_{2max} = -j \frac{V_1 \sqrt{R_o' R_i'}}{2 R_o' R_i'} = \frac{-j V_1}{2 \sqrt{R_o' R_i'}}$$

Magnitude is

$$|I_{2max}| = \frac{V_1}{2 \sqrt{R_o' R_i'}}$$

→ at \$\omega = \omega\_0\$ we have maximum power along with this frequencies there are two other frequencies for which \$I\_2\$ is maximum & can be obtained equating \$I\_{2max}\$ with \$I\_2\$ & resolving other 2 frequencies.

$$\left| \frac{-j V_1}{2 \sqrt{R_o' R_i'}} \right| = \left| \frac{-j V_1 \sqrt{R_o' R_i'}}{(R_o' + j\omega L + \frac{1}{j\omega C_L})(R_i' + j\omega L_2 + \frac{1}{j\omega C_2}) + b^2 R_o' R_i'} \right|$$

by putting \$k = b k\_c\$

$$L_2 = L$$

$$C_2 = C_1 = C$$

$$R_o' = R_i' = R$$

$$j(\omega L - \frac{1}{\omega C}) = jX$$

$$Z_{in} = \frac{-Z_{12}}{Z_{22}} = \frac{-j\omega M_c}{R_i' + j(\omega L_2 - \frac{1}{\omega C_2})}$$

at resonance \$\omega\_0 L = \frac{1}{\omega\_0 C} \Rightarrow \omega\_0 L\_2 = \frac{1}{\omega\_0 C\_2}\$

$$Z_{in} = \frac{\omega_0^2 M_c^2}{R_i'}$$

→ at resonance for maximum power transfer is at \$R\_o'\$ must be equal to \$Z\_{in}\$ i.e., \$M\$ is adjusted to critical value \$M\_c\$, such that

$$R_o' = \frac{\omega_0^2 M_c^2}{R_i'}$$

$$\therefore R_o' R_i' = \omega_0^2 M_c^2$$

$$\sqrt{R_o' R_i'} = \omega_0 k_c \sqrt{L L_2}$$

\$k\_c\$ is critical coefficient of coupling.

$$\therefore k_c = \frac{\sqrt{R_o' R_i'}}{\omega_0 \sqrt{L L_2}}$$

$$= \left( \frac{R_o'}{\omega_0 L} \right)^{1/2} \cdot \left( \frac{R_i'}{\omega_0 L_2} \right)^{1/2} = \frac{1}{\sqrt{Q_1 Q_2}}$$

In general \$k \neq k\_c\$.

& then let \$k = b k\_c\$.

To define the maximum gain w.r.t. maximum current consider the KVL equations.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$0 = Z_{21} I_1 + Z_{22} I_2$$

solving we get \$I\_2 = - \frac{V\_1 Z\_{21}}{Z\_{11} Z\_{22} - Z\_{21}^2}\$

$$\left| \frac{\tilde{V}_1}{2R} \right| = \frac{V_1 b R}{(R + jX)^2 + b^2 R^2}$$

$$|2bR^2| = |-X^2 + j2RX + R^2 + b^2 R^2|$$

Squaring on both sides & solving we get

$$4b^2 R^4 = [R^2(1+b^2) - X^2] + 4R^2 X^2$$

& solving for \$X\$, we get

$$X = \pm \sqrt{(b^2 - 1) \cdot R}$$

$$\therefore \omega L - \frac{1}{\omega C} = \pm \sqrt{(b^2 - 1) \cdot R}$$

$$\omega^2 LC - 1 = \pm \sqrt{(b^2 - 1) \cdot \omega CR} \rightarrow \textcircled{a}$$

On general \$Q\$ is large, so that

$$\omega CR \approx \omega_0 CR = \frac{1}{Q}$$

$$\& \text{ also } \omega_0 = \frac{1}{LC}$$

\$\therefore\$ eq. \$\textcircled{a}\$ can be rewritten as

$$\frac{\omega^2}{\omega_0^2} - 1 = \pm \frac{\sqrt{b^2 - 1}}{Q}$$

$$\frac{\omega^2}{\omega_0^2} = 1 \pm \frac{\sqrt{b^2 - 1}}{Q}$$

$$\omega \approx \pm \omega_0 \sqrt{1 \pm \frac{\sqrt{b^2 - 1}}{Q}}$$

→ If \$b < 1\$, coupling coefficient is less than the critical value then from above equation we find the \$\omega\$ becomes complex which leads to no real frequencies at which maximum power gets transferred.

maximum.

→ The 3-dB frequencies at which  $I_L$  reduces to 0.707 of its maximum value is lower & upper cut off frequencies can be obtained by.

$$\left| \frac{-j V_1 b \sqrt{R_0' R_1'}}{(R_0' + j\omega L + \frac{1}{j\omega C})(R_1' + j\omega L_2 + \frac{1}{j\omega C_2}) + b^2 R_0' R_1'} \right| = \frac{1}{\sqrt{2}} \left| \frac{-j V_1}{2 \sqrt{R_0' R_1'}} \right|$$

By applying the condition it can be reduced to.

$$\left| \frac{V_1 b R}{\frac{1}{2} (X + R)^2 + b^2 R^2} \right| = \frac{1}{\sqrt{2}} \left| \frac{V_1}{2 R} \right|$$

$$|2 \sqrt{2} b R^2| = | -X^2 + j 2 X R + R^2 + b^2 R^2 |$$

$$(b) \quad 8 b^2 R^4 = [R^2(1 + b^2) - X^2]^2 + 4 X^2 R^2$$

by solving

$$X = \pm \sqrt{(b^2 - 1 \pm 2b)} R$$

$$\omega L - \frac{1}{\omega C} = \pm \sqrt{b^2 - 1 \pm 2b} \cdot R$$

$$\omega^2 LC - 1 = \pm \sqrt{b^2 - 1 \pm 2b} \omega CR$$

$$\therefore \omega_0^2 = \frac{1}{LC} \text{ \& } \omega CR = \frac{1}{Q} \text{ Substituting}$$

$$\text{we get } \frac{\omega^2}{\omega_0^2} - 1 = \pm \frac{\sqrt{b^2 - 1 \pm 2b}}{Q}$$

Or by multiplying on both side with  $\omega_0$  we get  $\omega$  &  $\omega_0$  on the left side.

we get

$$\omega \omega_0 LC - \frac{\omega_0}{\omega} = \pm \sqrt{b^2 - 1 \pm 2b} \omega_0 CR$$

$$\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} = \pm \frac{\sqrt{b^2 - 1 \pm 2b}}{Q}$$

at <sup>two</sup> 3-dB frequencies  $\omega_2$  &  $\omega_1$ , one corresponds to a positive value & other for Negative sign.

→ Then

$$\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} = - \left[ \frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1} \right]$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

→ Taking +ve sign & Negative & solving we get

3-dB band as

$$(\omega_2 - \omega_1) = \sqrt{(b^2 - 1) \pm 2b} \cdot \frac{\omega_0}{Q}$$

→ BW is proportional to  $\frac{\omega_0}{Q}$

→ In a single-tuned amplifier  $BW = \frac{\omega_0}{Q}$ , in double-tuned is exceeds by a factor  $\sqrt{b^2 - 1 \pm 2b}$

→ If  $b < 0.414$  no real value of bandwidth &  $b$  should be only with

Positive sign.

→ If  $b < 2.414$  ~~also~~ yields four values of 3-dB freq. in practice.

→ So compromise value of  $b$  is kept in the range of 1 to 1.7

→ If  $b < 1$  leads to a steeper sides of the curve &  $b \gg 1$  is increased beyond the limit the overshoots of the frequency

response also increases.

\_\_\_\_\_ X \_\_\_\_\_